

**DATE: 28-APR-2021** 

## Lab Exercise - 3

COMPUTER ARCHITECTURE & ASSEMBLY LANGUAGE

Course: CSC-3402, Sec: 02

**Lecturer:** Dr. HAFIZAH BINTI

**MANSOR** 

## **Submitted by:**

Name: Hasan Tanveer Mahmood

Matric no: 1725413

## **Multicycle Processor Datapath**

 


Figure 1 addi instruction

RTL Statement for Figure 1: 1. IF; 2. IR = Memory[PC]; 3. PC = PC+4

 


Figure 2 xor instruction

RTL Statement for Figure 2:

- 1. ID
- 2. A = Reg[IR[25-21]], B = Reg[IR[20-16]]
- 3. ALUOut = PC + (sign-extend(IR[15-0] << 2)

 


Figure 3 beq Instruction

RTL Statement for Figure 3: 1. Execution Branch; 2. if(A==B) then PC =ALUOut

 


Figure 4 sw instruction

RTL Statement for Figure 4: 1. Memory access completion; 2. Memory[ALUOut] = B;

 


Figure 5 lw instruction

RTL Statement for Figure 5: 1. Memory read completion; 2. MDR = Memory[ALUOut];